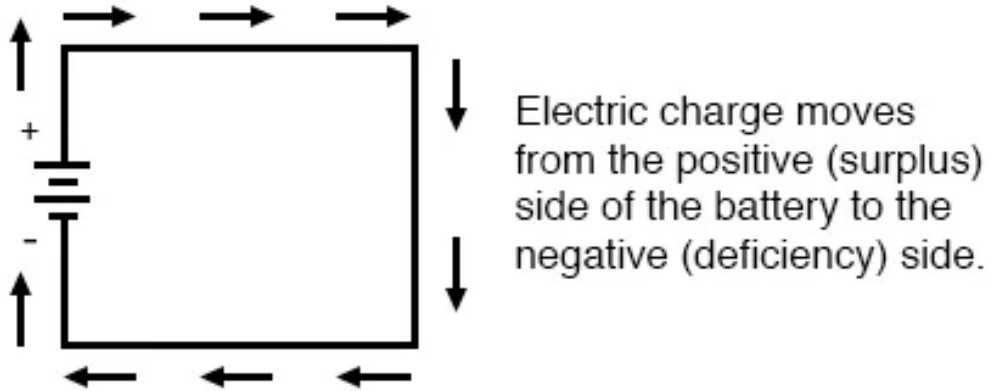



Intro to Electronics

Conventional Flow Notation



How it's notated

Electron Flow Notation

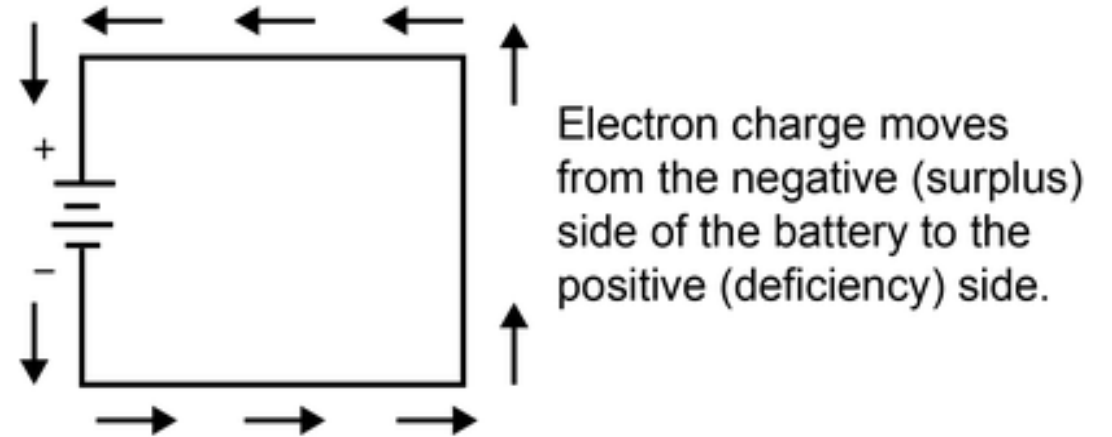

How it actually is

Electrons


<https://www.allaboutcircuits.com/textbook/direct-current/chpt-1/conventional-versus-electron-flow/>

AC / DC

Direct current for lower voltages
and running circuit boards

Alternating for higher power:
appliances, tube amps, etc.

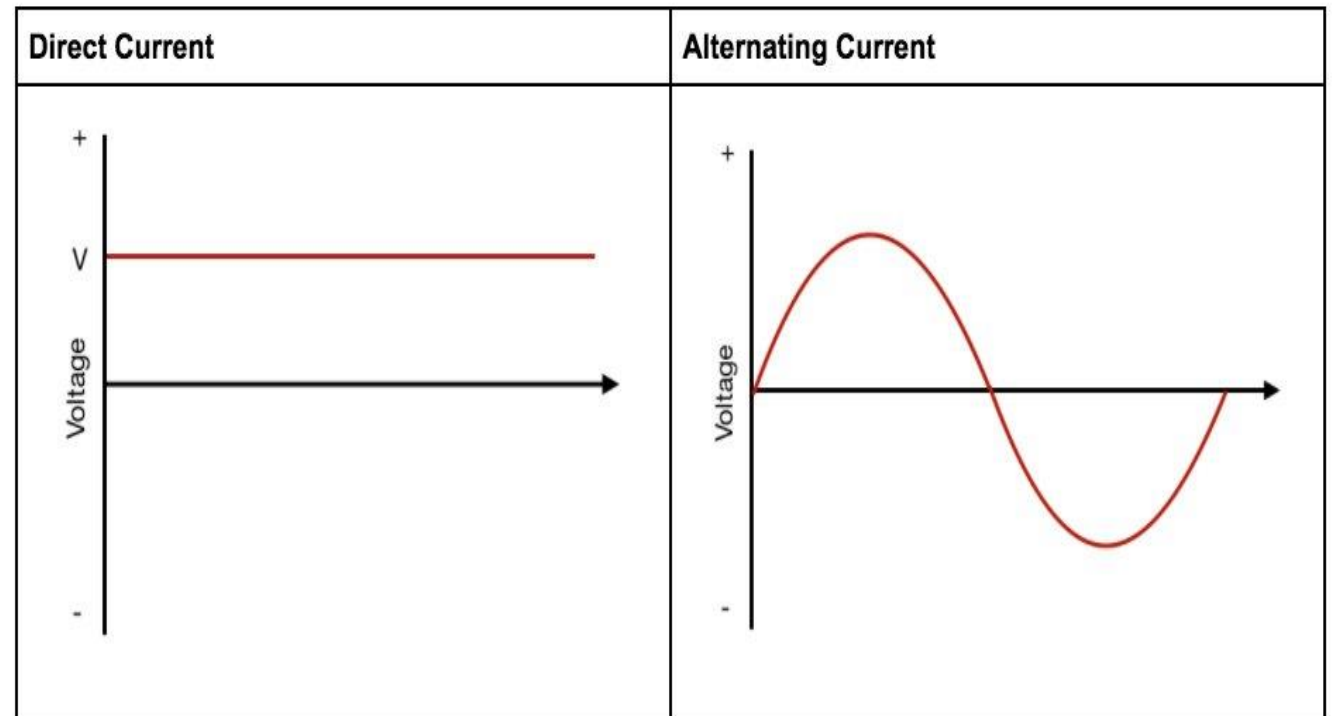Some circuits use a rectifier circuit
to change AC to DC



Ohm's Law

$$V = I * R$$

voltage = current * resistance


voltage = volts

current = amperes (amps)

resistance = ohms

Voltage is the pressure from an electrical circuit's power source that pushes charged electrons (current) through a conducting loop
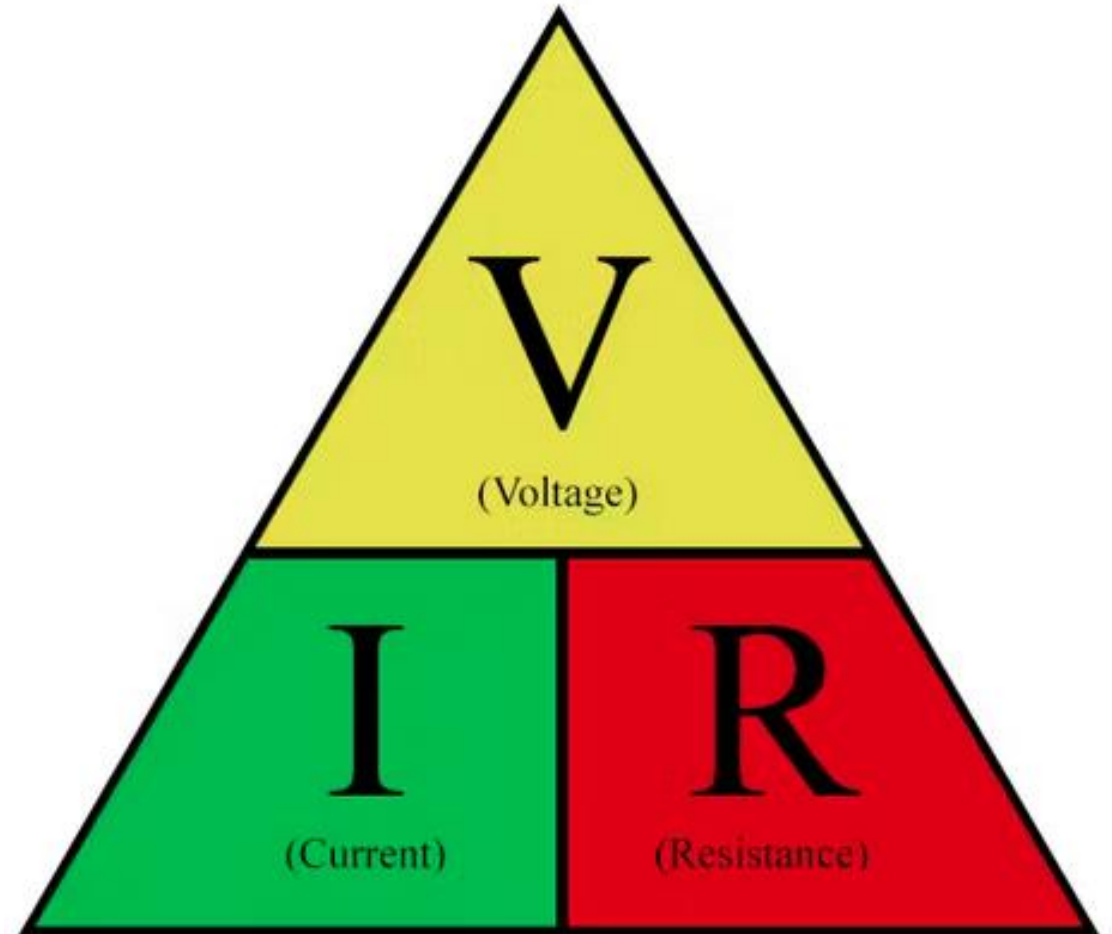
<https://www.fluke.com/en-us/learn/blog/electrical/what-is-voltage>



Conductors & Insulators


5 Electrical Conductors



silver



gold

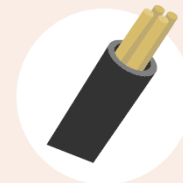

copper




steel



sea water

5 Electrical Insulators

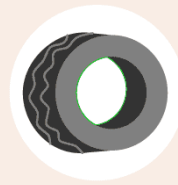

rubber



glass



oil



diamond




dry wood



Resistor



Diode

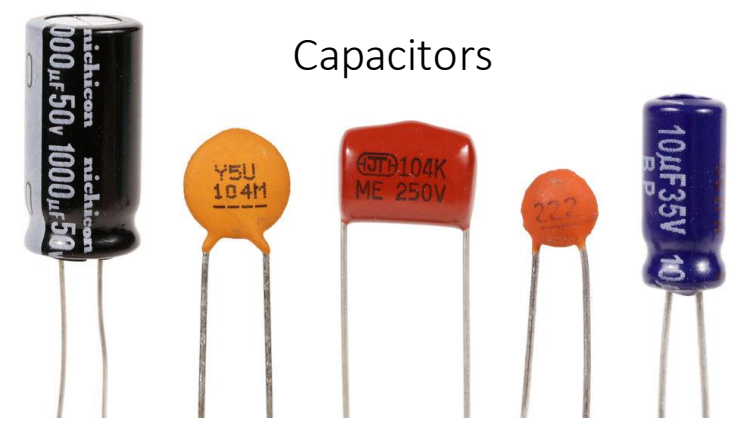

Capacitors

PHOTOCELL
(light-dependent resistor)


RHEOSTAT
(two-leg variable resistor)

FORCE-SENSITIVE RESISTOR
(aka FSR; two-leg var resistor)

THERMISTOR RESISTOR
(two-leg variable resistor)

ROTARY POTENTIOMETER
(three-leg variable resistor)

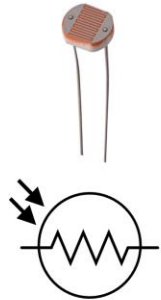SLIDE POTENTIOMETER
(three-leg variable resistor)




Light Emitting Diode (LED)



Some Electronics Parts

(... are polarized, some are not)

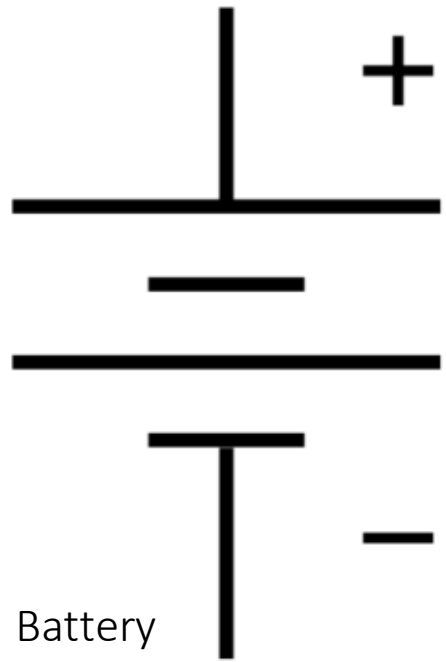

Battery



Resistor (2 symbols)



diode



light emitting diode

Non-polarized
Capacitor





Polarized
Capacitor



Some Schematic Symbols



Schematics, In General

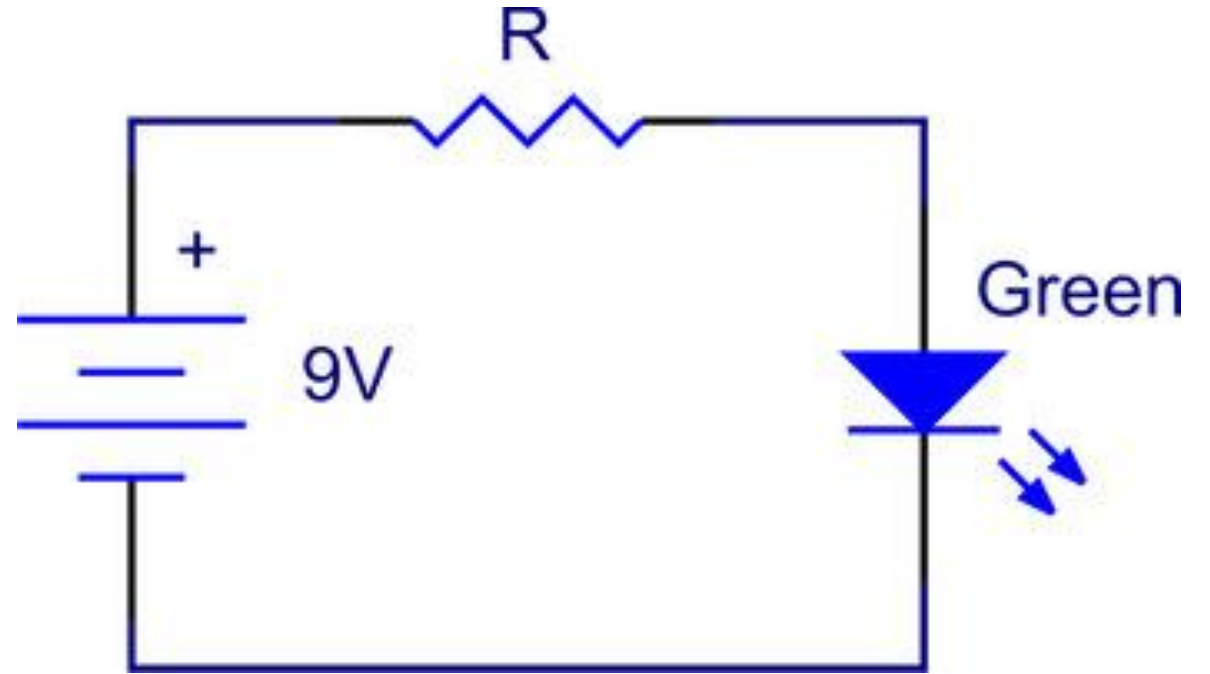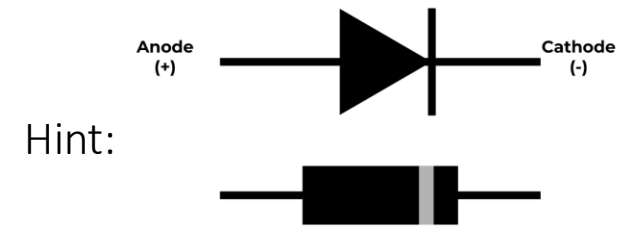

Tells you what is connected to what
But how to lay out the circuit on your
breadboard is up to you


Series and Parallel

Resistors: Series sums

Capacitors: Parallel sums


Otherwise, it's:
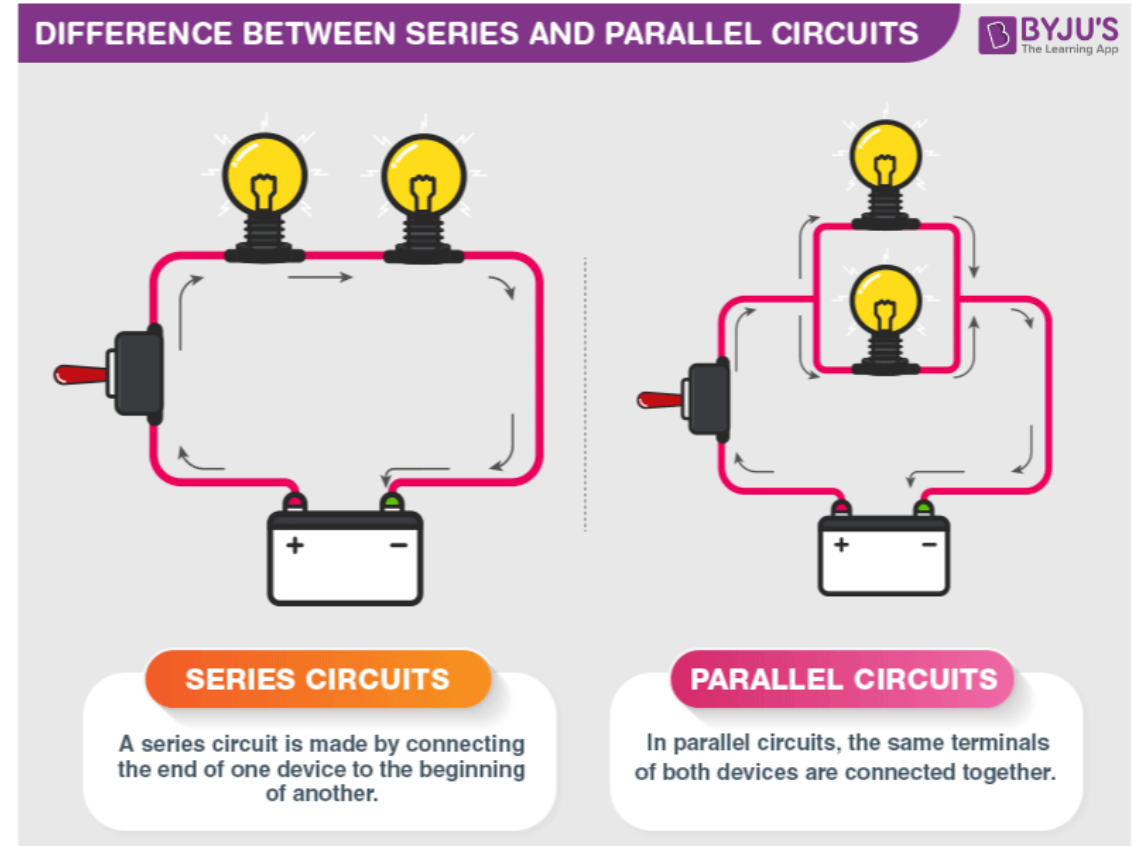
<https://learn.sparkfun.com/tutorials/capacitors/capacitors-in-seriesparallel>




Arduino : Digital I/O


Buttons and on/off signals

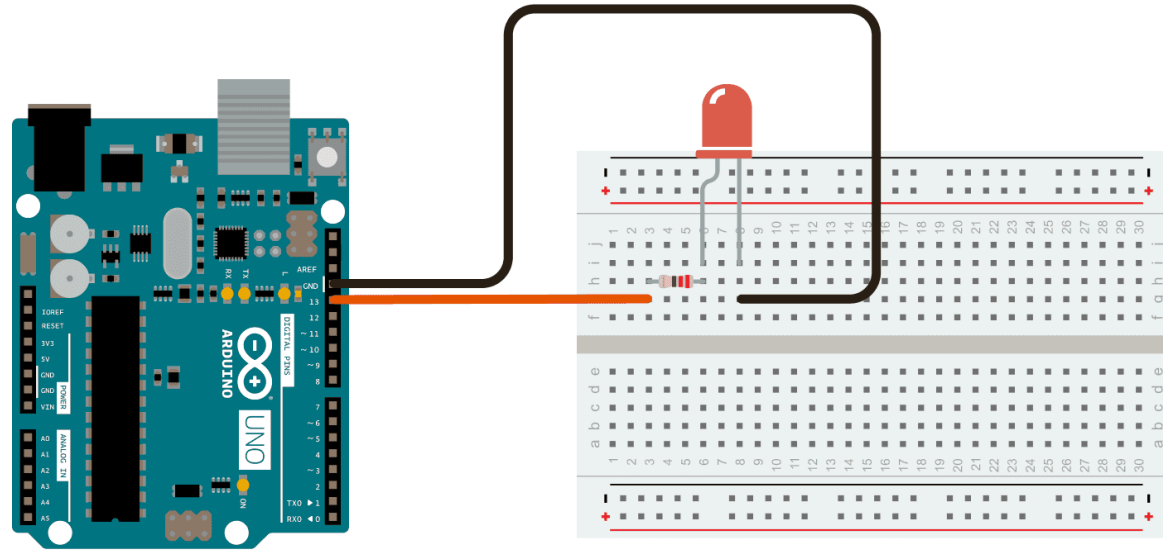

Arduino LED Wiring

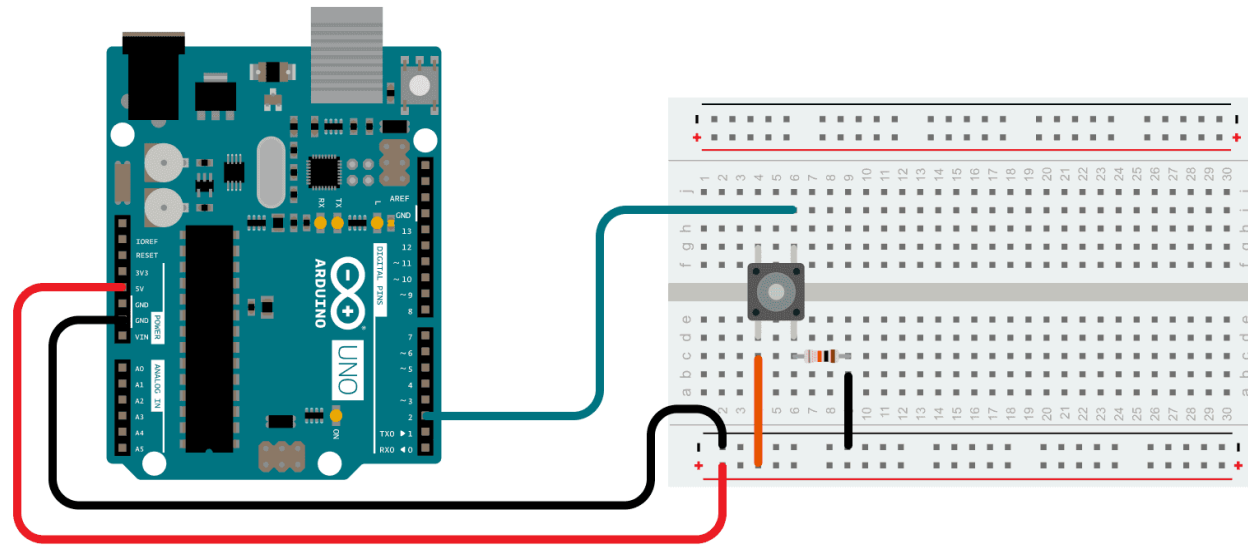


Arduino Button Wiring

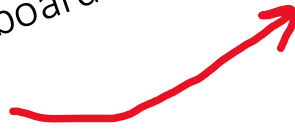


Arduino Button & LED Wiring

Analog I/O and PWM

Serial read and mapping

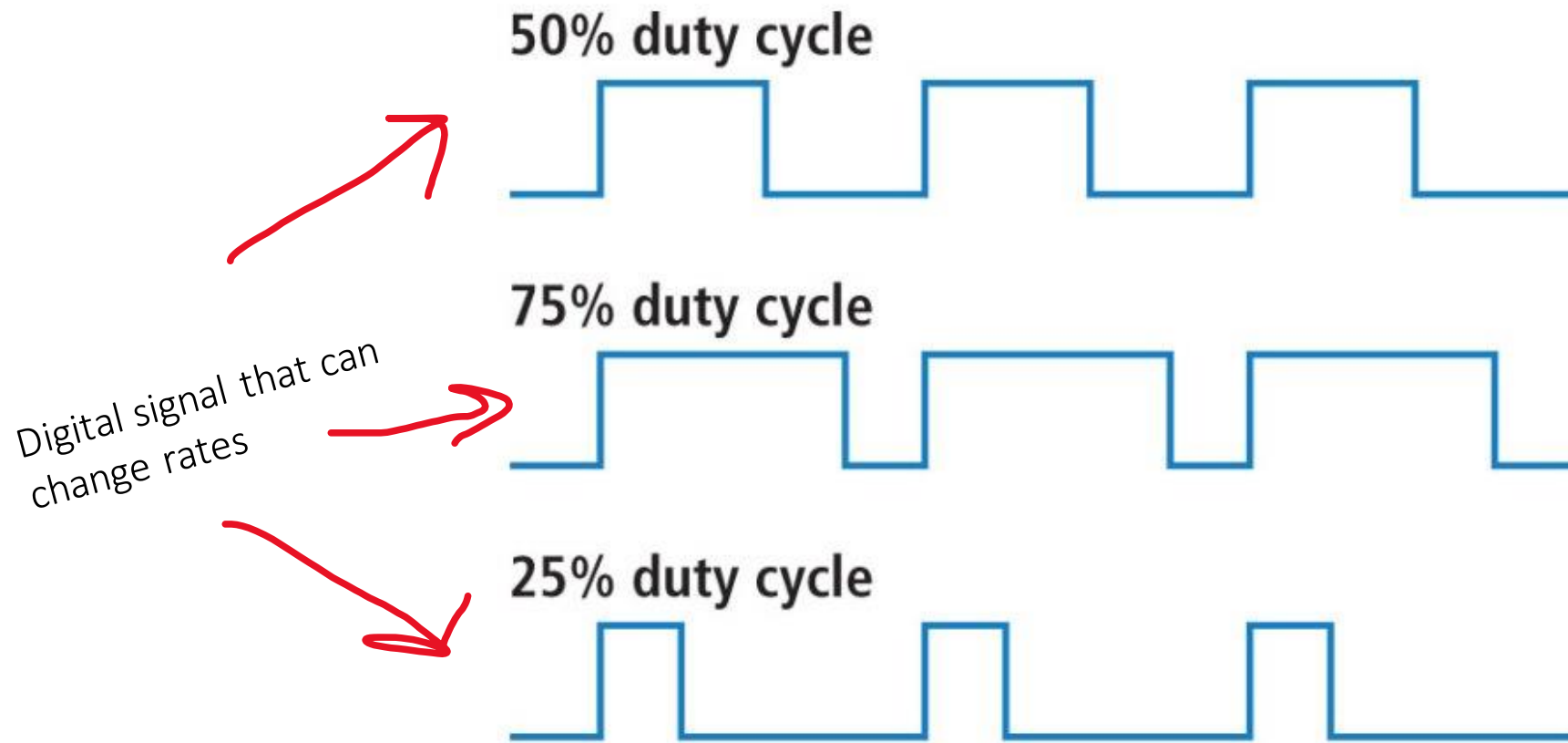


Pulse Width Modulation

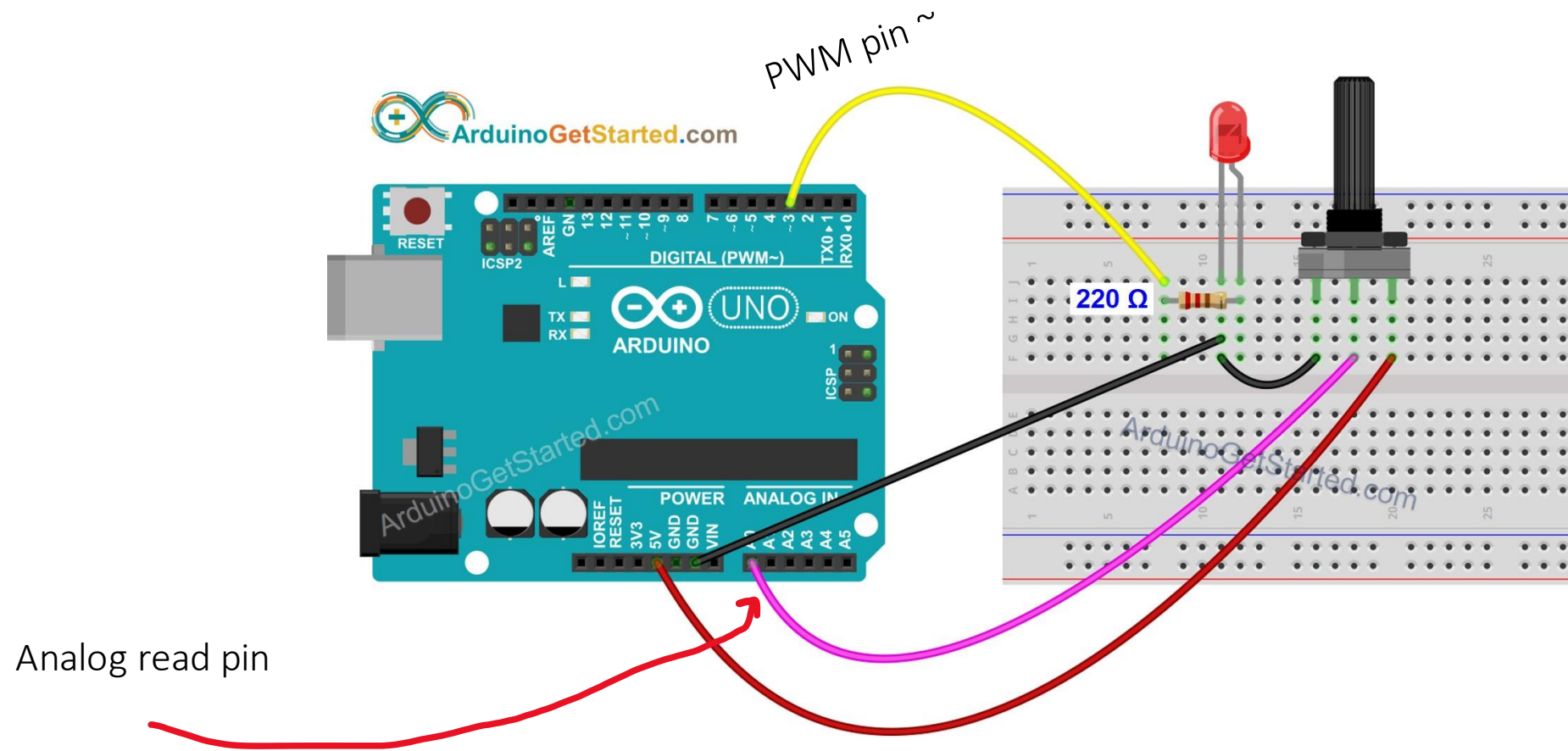


LED (PWM) and Knob (Analog)

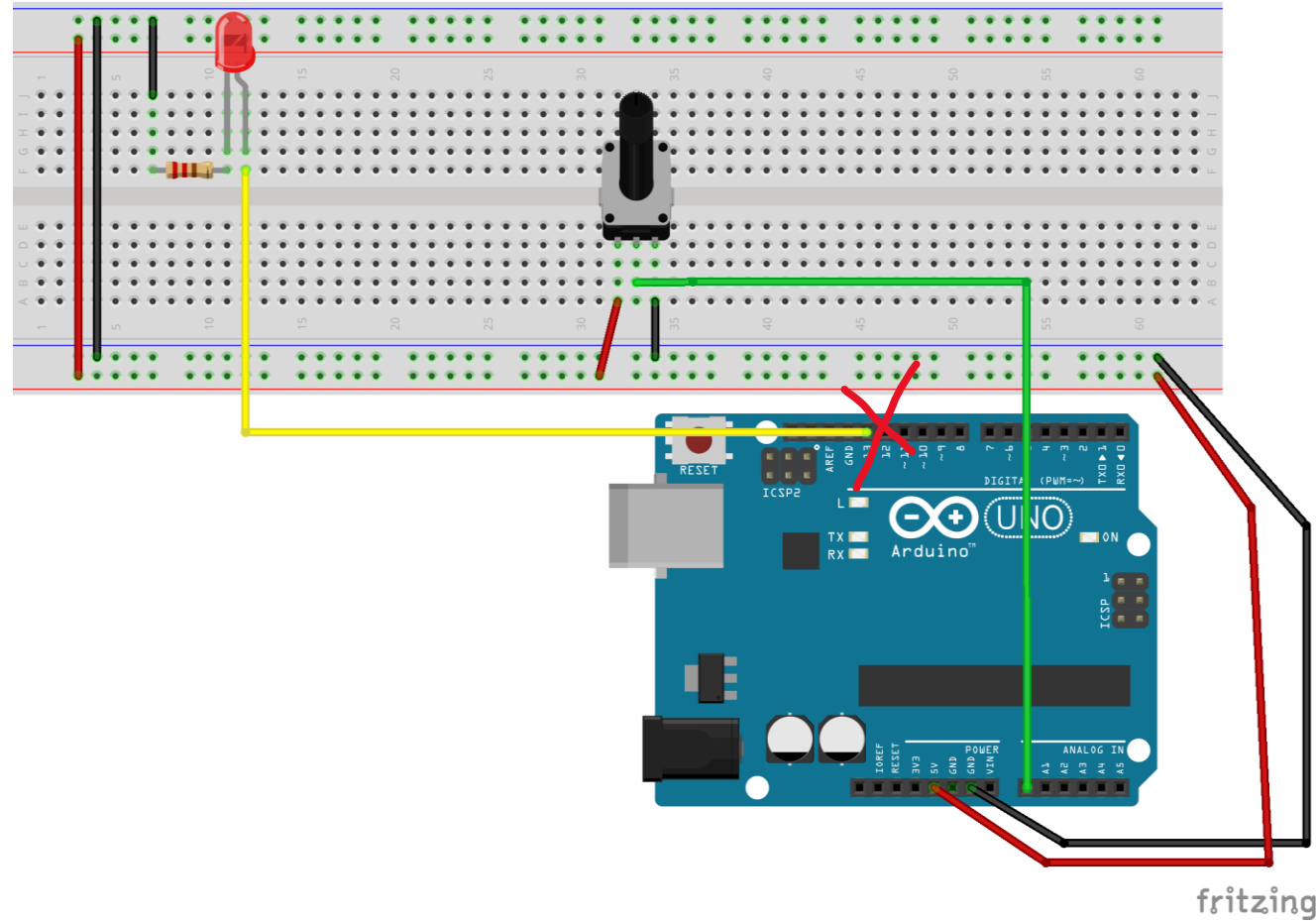Best practice to connect grounds to ground rail instead of to each other



Better Wiring, Pin 13 not PWM

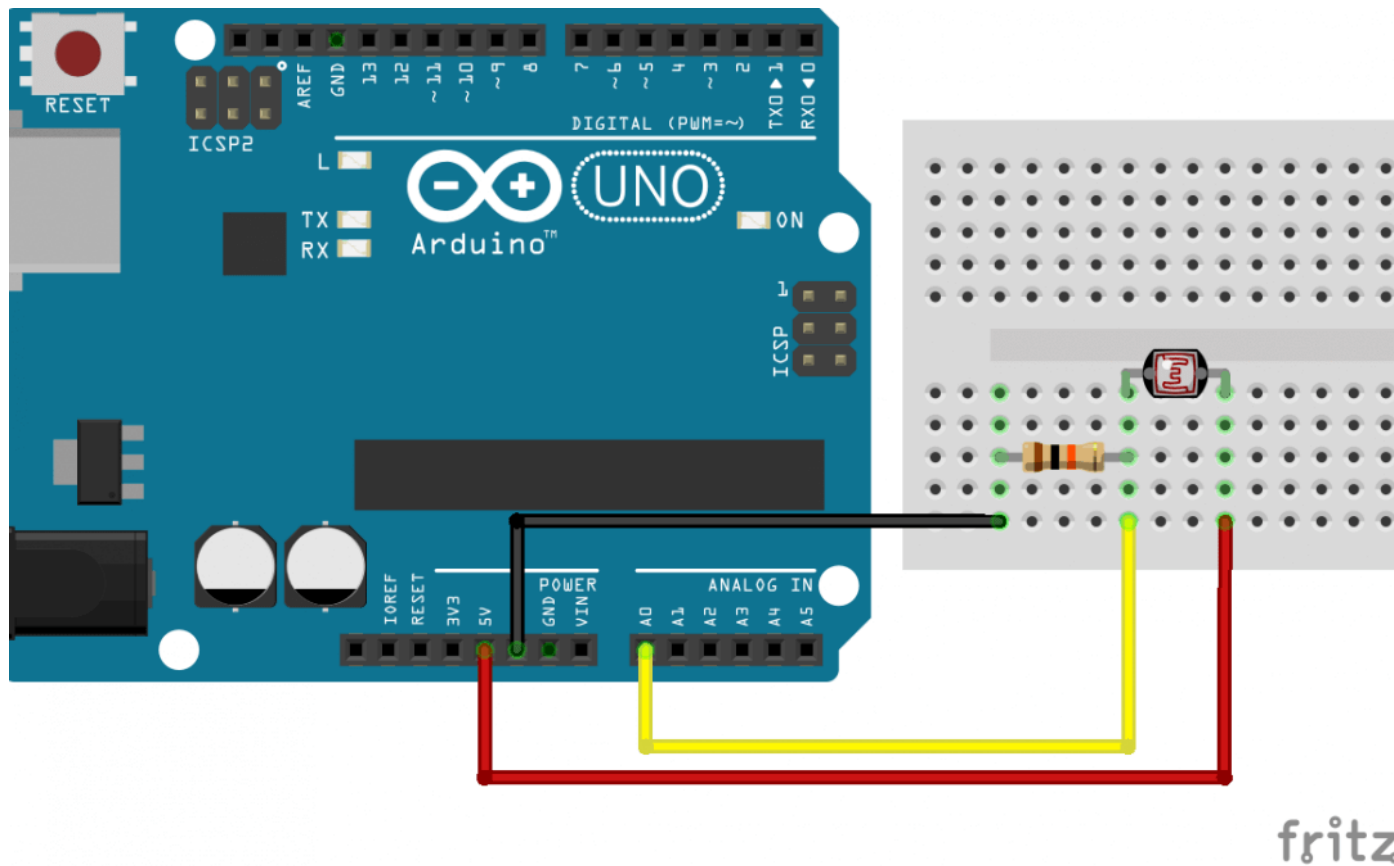

Create 3 pins to read
middle pin

Light-dependent Resistor (Analog)